

Register
Number

--	--	--	--	--	--	--

I Semester Diploma Examination, April/May-2017

CONCEPTS OF ELECTRICAL AND ELECTRONICS ENGINEERING

Time : 3 Hours]

[Max. Marks : 100

- Note :** (i) Answer any **six** questions from a set of 9 questions from Part-A. Each question carries 5 marks.
- (ii) Answer any **seven** questions from Part-B. Each question carries 10 marks.

PART – A

- | | |
|---|---|
| 1. Define : (i) Electric current
(ii) EMF. Write their units. | 5 |
| 2. State and explain Kirchhoff's current law. | 5 |
| 3. Define : (i) Amplitude
(ii) Frequency
(iii) RMS value
(iv) Average value
(v) Time period | 5 |
| 4. Define : (i) Self induced emf
(ii) Mutually induced emf | 5 |
| 5. What is rectifier ? List different types. | 5 |
| 6. Explain the function of a relay and list its applications. | 5 |
| 7. Write the block diagram of OP-AMP. | 5 |
| 8. What is the necessity of earthing ? List its types. | 5 |
| 9. Define switch. List types of switches with their symbols. | 5 |

PART – B

- | | |
|---|---|
| 10. (a) Define intrinsic semiconductor and extrinsic semiconductor. | 5 |
| (b) Explain the transistor as a switch. | 5 |
| 11. (a) State and explain Ohm's law. What are its limitations ? | 6 |
| (b) Explain : (i) Open circuit
(ii) Closed circuit. | 4 |

12. (a) Deduce an expression for effective resistance of two resistors connected in parallel. 5
- (b) A 100 watt lamp is used for 6 hours a day. Calculate
- (i) Energy consumed per month
- (ii) Cost of energy, if each unit costs ₹ 2.00 5
13. (a) State and explain Faraday's laws of electromagnetic induction. 5
- (b) Two resistances of $15\ \Omega$ & $10\ \Omega$ are connected in series, across a 50 V supply. Calculate
- (i) Effective resistance
- (ii) Total current in the circuit. 5
14. (a) Explain series R-L circuit. 5
- (b) Explain pure resistive circuit connected to A.C. source with waveform. 5
15. (a) Explain series R-C circuit. 5
- (b) Explain pure inductive circuit with waveform. 5
16. (a) Explain series R-L-C circuit and derive an expression for impedance. 6
- (b) A circuit consists of a resistance of $10\ \Omega$ and an inductance of 0.2 H. Find 4
- (i) Inductive reactance
- (ii) Impedance of the circuit, at 50 Hz frequency. 4
17. (a) Explain the working principle of transformer. 5
- (b) List the applications of transformer and stepper motor. 5
18. (a) Explain the operation of diode and draw VI characteristics. 6
- (b) Write the block diagram of UPS. 4
19. (a) Explain OP-AMP as inverting amplifier. 5
- (b) What are the precautions to be taken in the maintenance of lead acid battery? 5