

1188

Code : 15EC01T

Register
Number

--	--	--	--	--	--	--

I Semester Diploma Examination, Nov./Dec. 2017

CONCEPTS OF ELECTRICAL & ELECTRONICS ENGINEERING

Time : 3 Hours |

| Max. Marks : 100

- Note :** (i) Answer any **six** questions from **Part-A**. Each question carries **5**-marks.
(ii) Answer any **seven** questions from **Part-B**. Each question carries **10**-marks.

PART-A

1. Define electric current, voltage and resistance. Write their SI units. 5
2. State and explain Kirchoff's current law. 5
3. Define : 5
 - (i) MMF
 - (ii) Reluctance
4. Explain RMS value and average value. 5
5. An alternating current has a maximum value of current is 25 A. Find RMS value, average value, form-factor and crest-factor. 5
6. Explain the construction of transformer. 5
7. Explain the need of spike busters for protection of computers. 5
8. Define conductor, semi-conductor and insulator. 5
9. Explain the working of C-filter. 5

PART-B

10. (a) Distinguish between series and parallel resistor circuits. 5
(b) Two resistors of 10Ω and 20Ω are connected in series across 20 V supply. 5
Find :
(i) Effective resistance of the circuit.
(ii) Total current in the circuit.
11. (a) Compute the total resistance of parallel combination of resistors. 5
(b) Three resistance of 2Ω , 4Ω , 16Ω are connected parallel across 50 V supply. 5
Calculate total resistance and total current.
12. (a) Distinguish between electric circuit and magnetic circuit. 5
(b) Write the applications of the stepper motor. 5
13. (a) Define the following terms with respect to sinusoidal wave : 6
(i) Phase-difference
(ii) In-phase
(iii) Out-off-phase
(b) Calculate capacitive reactance and power factor in RC series circuit with 4
 $C = 10\ \mu\text{F}$, $R = 100\ \Omega$ & $f = 50\ \text{Hz}$.
14. (a) Define power factor and impedance with respect to AC. Write their units. 5
(b) Compute the expression that, the current I leads the voltage V by 90° ($\pi/2$), 5
when AC flows through capacitor.
15. Analyze the behaviour of series RLC circuit for AC input. 10
16. (a) What is necessity of earthing ? Mention its type. 5
(b) Explain working principle of relay. 5
17. (a) List ideal characteristics of Op-Amp. 5
(b) With a neat circuit diagram, explain the working of Op-Amp inverting 5
amplifier.
18. (a) What is transistor ? Mention different types of transistor with their symbols. 4
(b) Explain V-I characteristics of forward biased PN junction diode. 6
19. (a) Explain UPS with block diagram. 6
(b) Name different type of batteries. 4