

1303**Code : 15EC01T**Register
Number

--	--	--	--	--	--	--

I Semester Diploma Examination, Nov./Dec. 2016**CONCEPTS OF ELECTRICAL AND ELECTRONICS
ENGINEERING****Time : 3 Hours]****[Max. Marks : 100**

- Note :** (i) Answer any **six** questions from Part – A.
(ii) Answer any **seven** questions from Part – B.

PART – A

1. Define the following and write their SI units :

5

- (i) Electric current
(ii) EMF

2. State Kirchhoff's laws.

5

3. Define the following with SI units :

5

- (i) Amplitude
(ii) Time period

4. List out the differences between single phase and three phase ac supply.

5

5. A 10 kVA, 2200/220 Volts, single phase transformer has 60 turns on secondary.
Determine the

5

- (i) No. of turns on primary and
(ii) Secondary current

[1 of 4]**[Turn over**

6. Explain the method of protecting computer from power transients. **5**
7. Differentiate conductors, insulators and semiconductors. Give one example for each. **5**
8. Explain UPS with a block diagram. **5**
9. State Faraday's laws of electromagnetic induction. **5**

PART – B

10. (a) A resistance of $6\ \Omega$ is connected in series with a parallel combination of $30\ \Omega$ and $20\ \Omega$ resistances. This combination is connected across $36\ \text{V}$ supply.

Calculate :

7

- (i) Total resistance
- (ii) Branch currents
- (iii) Total current

- (b) Explain open, close and short circuit conditions. **3**

11. (a) Explain self induced emf.

- (b) Explain generation of alternating current. **5**

12. (a) If an alternating current is given by $i = 100 \sin 314 t$ find **5**

- (i) Maximum value
- (ii) Frequency
- (iii) RMS value
- (iv) Average value

- (b) Define : **5**

- (i) RMS value
- (ii) Average value of an alternating current

13. (a) For a series RC circuit connected across ac supply. Write the sketch of circuit diagram and vector diagram. Also, write the expressions for voltage, current, impedance and power factor. **6**
- (b) For a series RLC circuit with $L = 60 \text{ mH}$, $C = 50 \mu\text{F}$ and $R = 6 \Omega$. Calculate the impedance of the circuit. Assume $f = 50 \text{ Hz}$. **4**
14. (a) A series RL circuit with $R = 20 \Omega$, $L = 20 \text{ mH}$ is connected across 230 V , 50 Hz ac supply. Determine the values of : **8**
- (i) Impedance
- (ii) Current
- (iii) Power factor
- (iv) Power
- (b) Define power factor.
15. (a) Explain : **5**
- (i) Current Ratio and
- (ii) Voltage Ratio of single phase transformer
- (b) What is an earthing ? Explain its necessity. List the types. **5**
16. (a) Explain the necessity of antistatic device and write the types of antistatic devices for protection of computers. **5**
- (b) Explain the criteria for selection of UPS. **5**
17. (a) Explain VI characteristics of PN junction diode. **5**
- (b) List the types of transistors. Write their symbols and mention applications. **5**

[Turn over

18. (a) Explain with a neat sketch the operations of Bridge rectifier. Also, draw the input and output waveforms. 6
- (b) List out the characteristics of Op-Amp. 4
19. (a) Explain with a neat sketch the operation of transistor as a switch. 6
- (b) Explain the procedure to maintain a battery. 4
-

BETA CONSOLE!

Diploma - [All Branches]

Beta Console Education



Diploma Question Papers [2015-19]

Beta Console Education

