

**1455****Code : 15EC-01T**Register  
Number

--	--	--	--	--	--	--

**I Semester Diploma Examination, April/May-2016****CONCEPTS OF ELECTRICAL & ELECTRONICS  
ENGINEERING****Time : 3 Hours ]****[ Max. Marks : 100**

- Note :** (i) Answer any **six** questions from Part-A. Each questions carries **5** marks.  
(ii) Answer any **seven** questions from Part-B. Each questions carries **10** marks.

**PART - A**

1. State and explain Ohm's law. Mention its limitations. **5**
2. Define electrical power and energy and the meters used to measure them. **5**
3. Define magnetic field and flux density. What is the unit of flux density ? **5**
4. Sketch AC voltage waveform and mark the parameters given below : **5**
  - (a) Instantaneous value
  - (b) Amplitude
  - (c) Time period
  - (d) Cycle
5. Differentiate between single phase and three phase AC supply. **5**
6. List the types of transformers and write their applications. **5**
7. What do you mean by a switch ? Classify the switches based on their operation. **5**
8. Define conductors, semiconductors and insulators with examples. **5**
9. What is an Op-Amp ? List the ideal characteristics of OP-AMP. **5**

## PART - B

10. (a) Explain open, closed and short circuit. 6  
(b) Define :  
(i) Current  
(ii) Emf and mention their units. 4
11. (a) Explain working principle of a relay. 5  
(b) What is the necessity of earthing ? Write the types of earthing. 5
12. (a) Explain self induced emf and mutually induced emf. 5  
(b) Define inductive reactance and capacitive reactance and mention their units. 5
13. (a) Define the following : 6  
(i) RMS value  
(ii) Average value  
(iii) Form factor  
(b) Bring out the comparison between DC and AC supply. 4
14. (a) Explain pure inductive AC circuit with waveform and vector diagram. 4  
(b) In an R-L series circuit,  $R = 30 \Omega$  and  $L = 0.5 \text{ H}$  are connected across 230 V, 50 Hz AC supply. Find  
(i) Impedance  
(ii) Current  
(iii) Power factor 6
15. (a) An AC voltage is given by  $v = 100 \sin 314 t$ , what is the maximum voltage and frequency ? 5  
(b) Define power and power factor and write their units. 5
16. (a) Explain the working principle of stepper motor. 5  
(b) Explain intrinsic and extrinsic semiconductor. 5
17. (a) What is a rectifier ? Explain half wave rectifier with a circuit and waveforms. 5  
(b) Sketch and explain V-I characteristics of PN Junction diode. 5
18. (a) Explain transistor as a switch. 5  
(b) What are filters ? List the types of filters. 5
19. (a) Explain working of SMPS with block diagram. 6  
(b) Name different type of batteries and write their applications. 4