

2656**Code : 15EC01T**Register
Number

--	--	--	--	--	--	--

I Semester Diploma Examination, Nov./Dec. 2015**CONCEPTS OF ELECTRICAL AND ELECTRONICS
ENGINEERING****Time : 3 Hours]****[Max. Marks : 100**

- Note :**
- (i) Answer any **six** questions from a set of **9** questions from Part – **A**, each question carries **5** marks.
 - (ii) Answer any **seven** questions from a set of **10** questions from Part – **B** each question carries **10** marks.

BETA CONSOLE!**PART – A**

1. Define electric power and energy. Mention their practical units. **5**
2. State Ohm's law and write the three equations of Ohm's law. **5**
3. State and explain Faraday's laws of electromagnetic induction. **5**
4. Draw an AC waveform and mark, instantaneous values, amplitude, time period and frequency on it. **5**
5. Define a power factor and explain lagging and leading power factor. **5**
6. A single phase 50 Hz, 11000/440 V transformer has 100 turns on the secondary, find the primary turns and it draws 10 Amps of current from supply, find the secondary current. **5**
7. Explain protection of computer systems against power transients. **5**
8. What is a transistor and mention the types of transistor with symbols. **5**
9. Define an Op-Amp and explain Op-Amp as an inverting amplifier. **5**

[Turn over

PART – B

10. (a) Define electric current, EMF and resistance with their units. 6
(b) Derive an equation for equivalent resistance, when three resistors are connected in parallel. 4
11. (a) A resistance of $5\ \Omega$ is connected in series with another resistance of $20\ \Omega$. Find the effective resistance and total current in the circuit, if it is connected across a 200 V supply. 4
(b) Define the following and mention their units : 6
• Magnetic flux
• MMF
• Reluctance
12. (a) Differentiate between single phase and three phase AC supply. 5
(b) Show that power consumed by a pure capacitive circuit is zero, along with waveforms and vector diagram. 5
13. (a) Define impedance, inductive reactance and capacitive reactance. 6
(b) An AC circuit consists of a resistance of $10\ \Omega$, an inductance of $0.15\ \text{H}$ in series. If this is connected across an AC supply of 250 V, 60 Hz, find the power consumed. 4
14. (a) List the applications of a stepper motor and spindle motor. 6
(b) Define RMS value and average value of an AC voltage. 4
15. (a) What is a switch and list the types of switches with symbols. 6
(b) What is a fuse ? Mention the types and ratings of fuse. 4
16. (a) Define conductors, semiconductors and insulators with an examples. 6
(b) Explain intrinsic and extrinsic semi conductors. 4
17. (a) What is a rectifier ? Explain the working of a centre tapped full-wave rectifier with waveforms. 6
(b) What is a filter ? Explain 'C' type filter. 4
18. (a) Explain the operation of a PN-junction diode with neat sketches. 5
(b) List the characteristics of an ideal Op-Amp. 5
19. (a) Define UPS and explain the block diagram of UPS. 5
(b) Explain the maintenance of a battery. 5
-